

Name:

Grade:

/10

- [10] 1) The following sequential circuit has two negative-edge-triggered flip-flops. Complete the timing diagram and clearly indicate the level changes at every clock transition.

